
EECS 413 LAB3

Hsiang-Yang Fan

1. Schematic of circuit

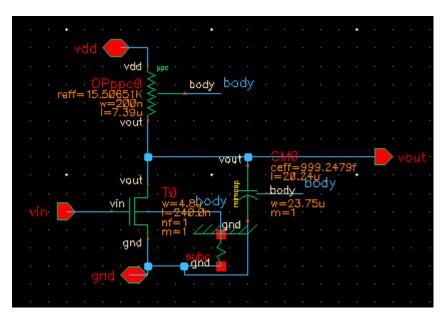


2. Explanation of design process

```
assume I_0 = 6t.5\mu A, "VGS >Vth & Vps > (VGS - Vth)

\Rightarrow V_{GS} = V_G - V_S = 0.4V, V_{GS} - V_{Th} = 0.1V, V_{DS} = 0.2V
I_0 = \frac{1}{2}\mu_1 G_X \left(\frac{V}{L}\right) \left(V_{GS} - V_{Th}\right)^2
\Rightarrow 64.5\mu = \frac{1}{2} \times 645 \mu \times \left(\frac{W}{L}\right) \left(0.4 - 0.3\right)^2
\Rightarrow \left(\frac{W}{L}\right) = 20 \mu
R = \frac{V_{DD} - V_D}{I_D} = 15.5 \text{K}_{D} + \frac{1}{2} \mu
S_M = M_1 G_X \times V_{GS} - V_{Th} = 6t.5 \times 10^{-6} \times 20 \times 0.1 = 1.29 \text{ m}
V_0 = -\frac{1}{2}\mu_1 = 51.7 \text{k}_D
\Rightarrow V_0 = -6t.5 \times 10^{-6} \times 20 \times 0.1 \times 11.9 \times 10^3 \text{ V}_{2S} = -15.35 \text{ V}_{2S}
\Rightarrow |A_V| = 20 \log 15.35 = 23.7 \text{d}_B
```


3. AC magnitude of schematic

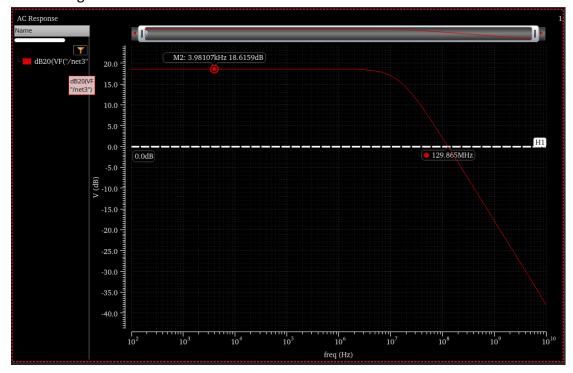


4. 3dB bandwidth of schematic

Value
15.27E6


5. I_D current of schematic

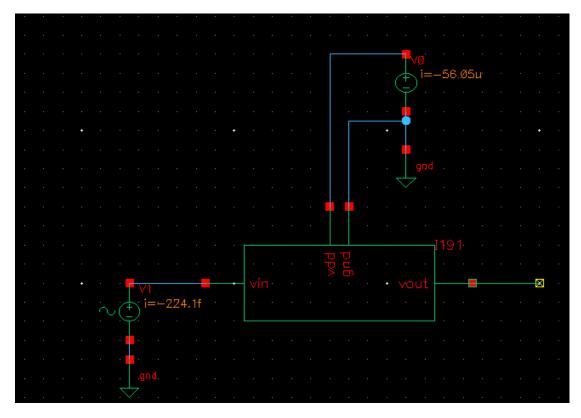


6. Layout

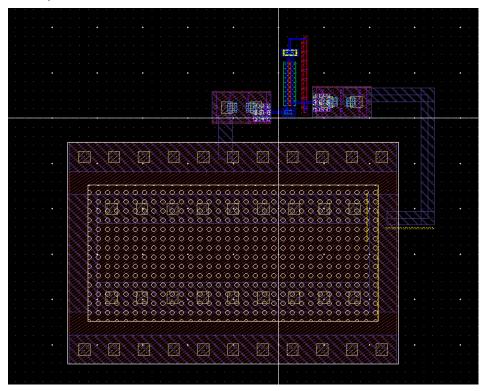


7. Clean DRC

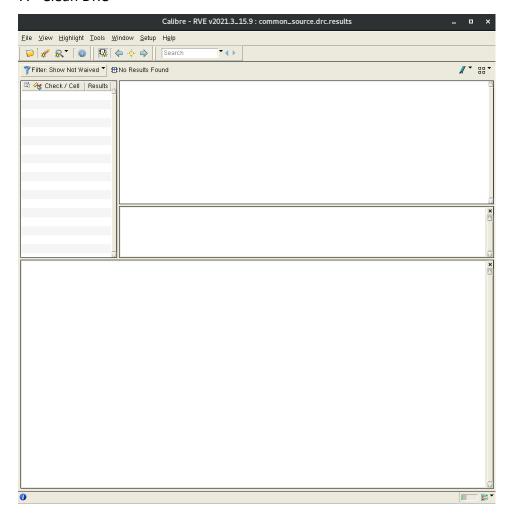

8. Clean LVS

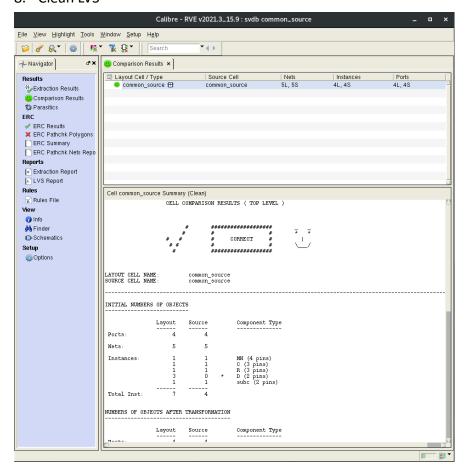

9. AC magnitude of postpex

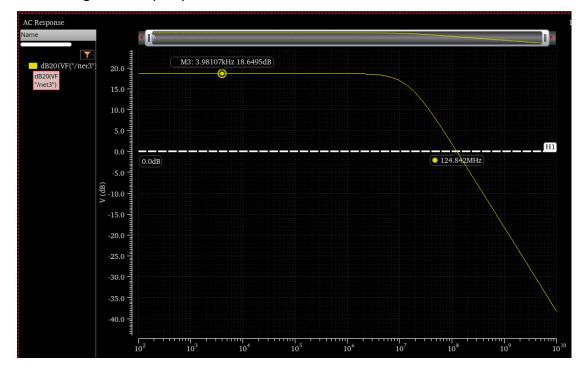

10. 3dB bandwidth of postpex

_ Expression	Value
1 bandwidth(VF("/	14.68E6

11. I_D current of postpex

